



ELECTRICITY

# The Basics

**Ohm's Law –  $I = V/R$**

I – current (amperes/amps)

V – voltage (volts)

R – resistance (ohms)




Voltage: a force that pushes the current through the circuit

Resistance: friction that impedes flow of current through the circuit

Current: the actual “substance” that is flowing through the wires of the circuit (electrons)
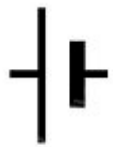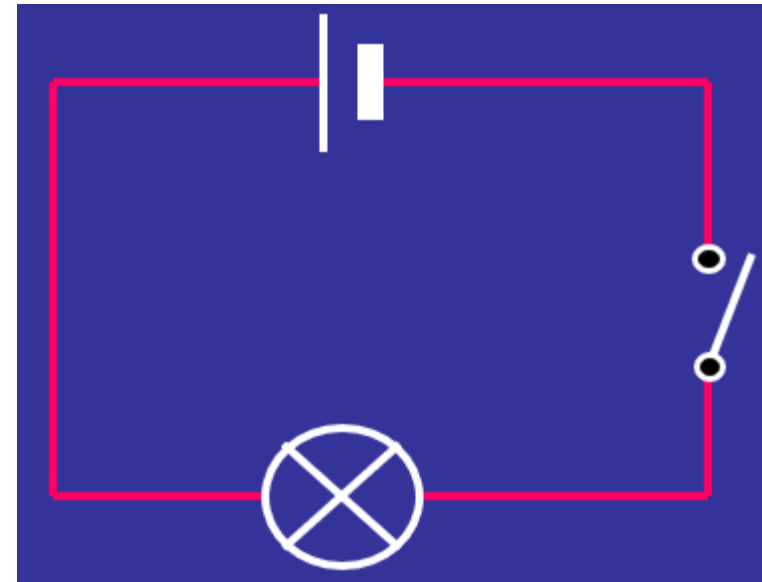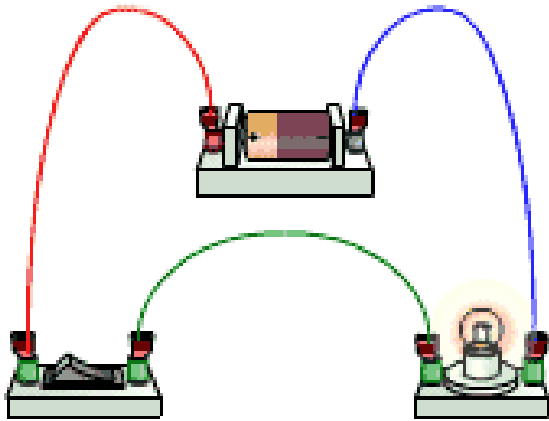
# Circuit Diagram

Scientists usually draw electric circuits using symbols:



cell



lamp



switch (open)




switch (closed)


# Simple Circuits

- Series circuit
  - All in a row
  - 1 path for electricity
  - 1 light goes out and the circuit is broken
  - Voltage is shared between the components
- Parallel circuit
  - Many paths for electricity
  - 1 light goes out and the others stay on
  - Voltage is the same in all parts of the circuit (for all components)

Series circuit


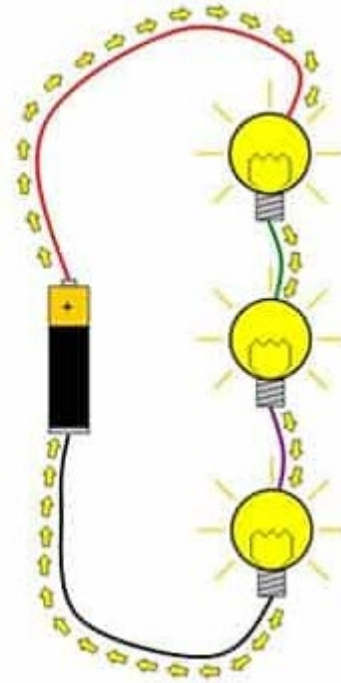


Parallel circuit

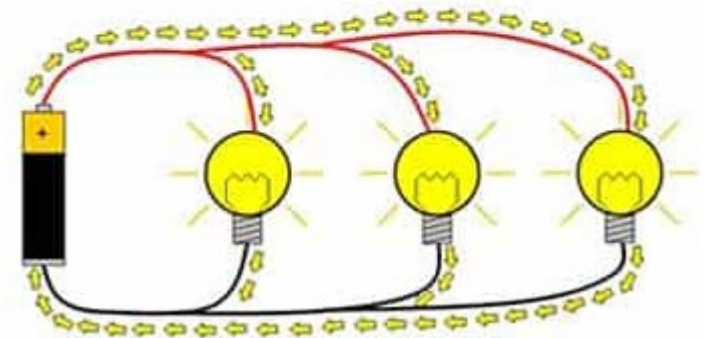

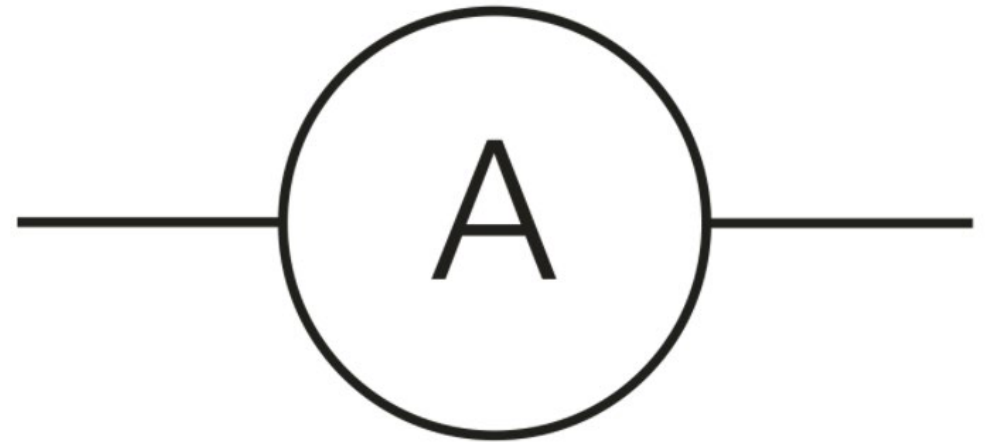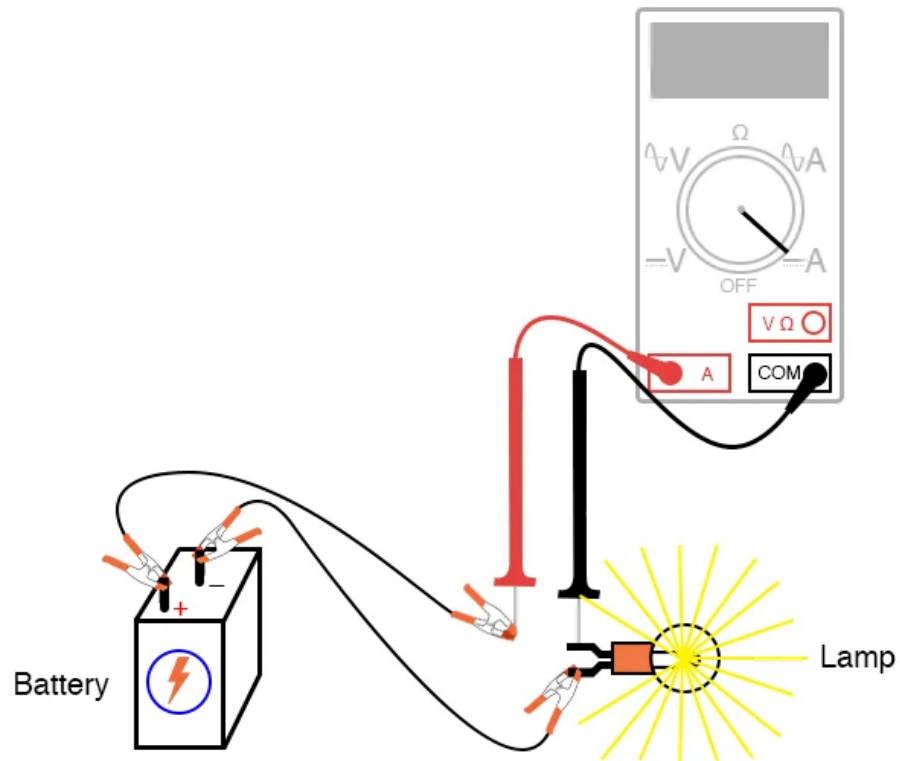
# Measuring Current


Electric current is measured in amps (A) using an ammeter connected in series in the circuit.



# An Ammeter in a Circuit

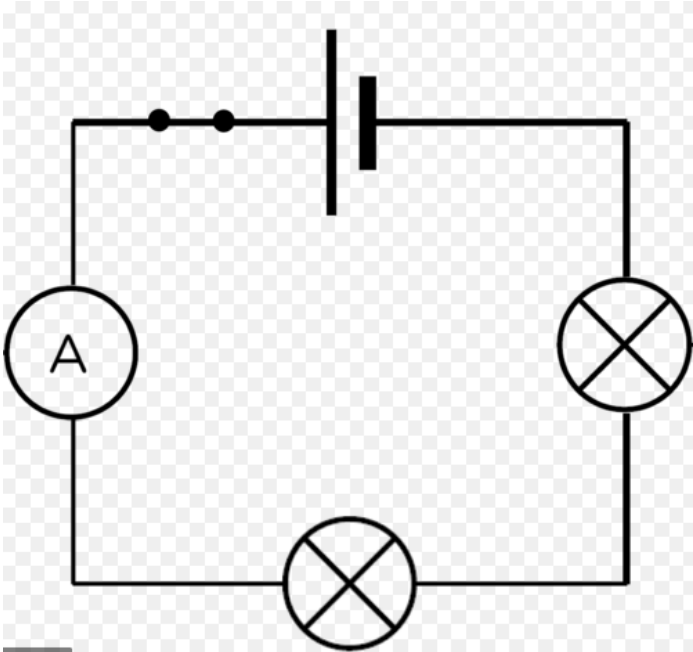


Series Circuit

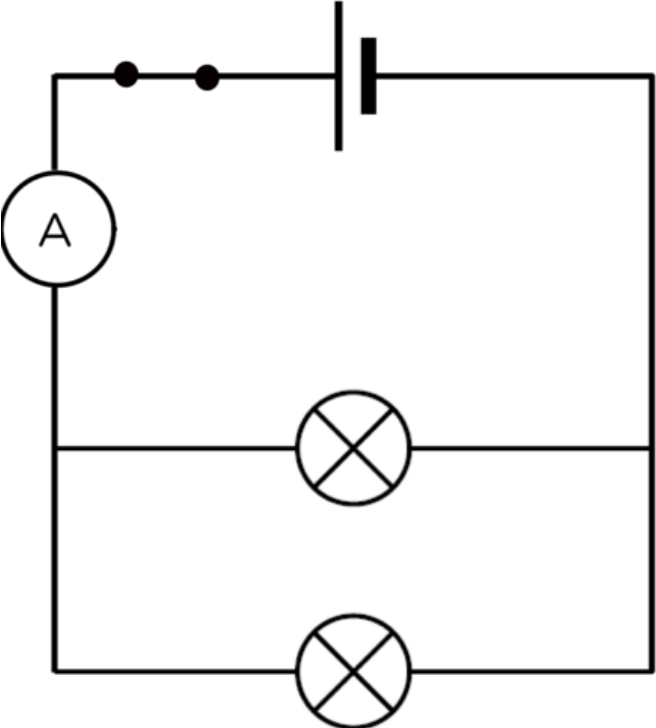

Parallel Circuit

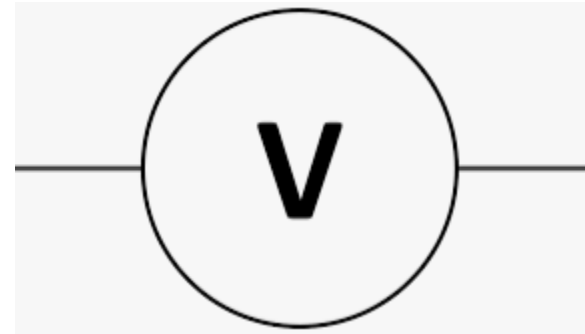
# Measuring Voltage

The 'electrical push' which the cell gives to the current is called the voltage. It is measured in volts (V) on a voltmeter.



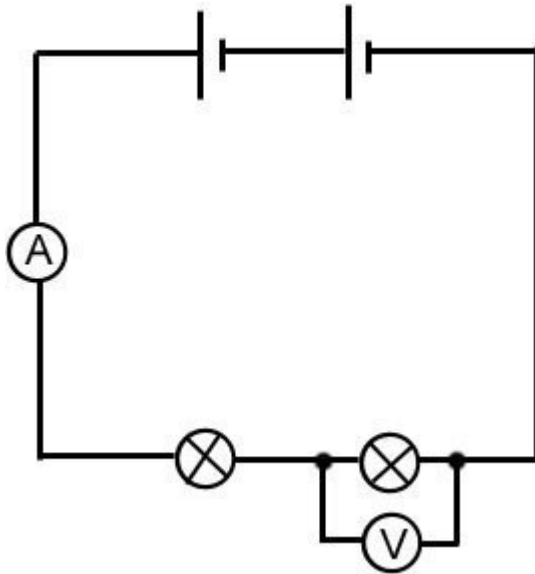
# Measuring Voltage


This is how to draw a voltmeter in a circuit.



Series Circuit

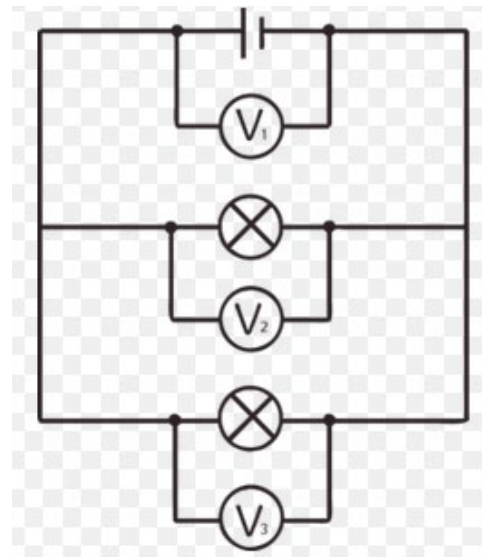

Parallel Circuit

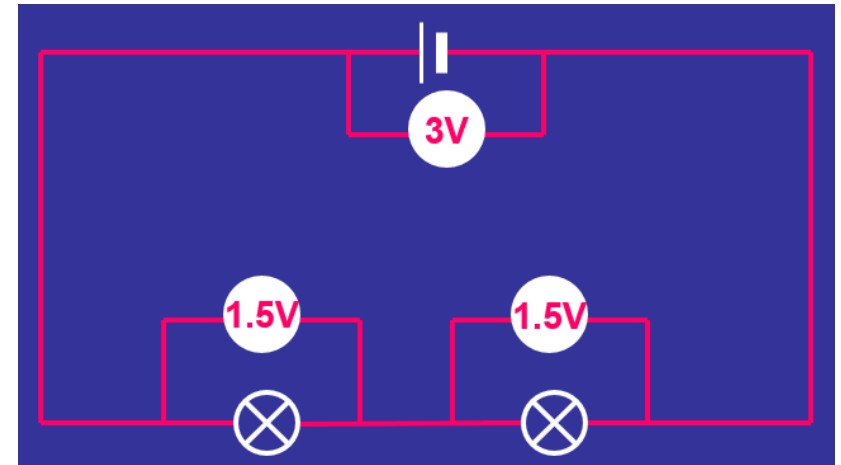


Series Circuit (voltage shared)



# Measuring Current

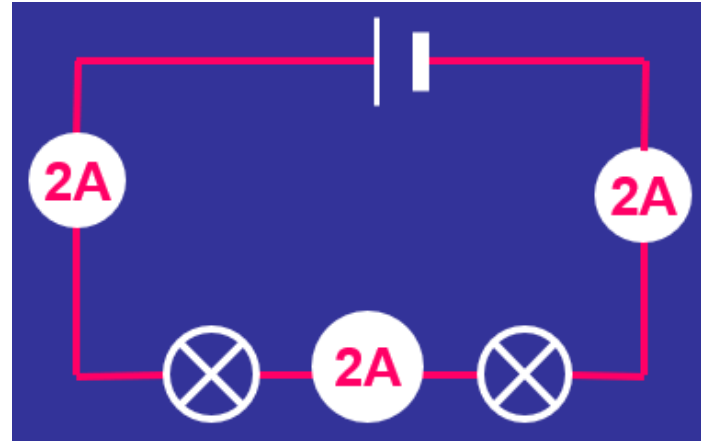
## Series Circuit

Current is the same at all points in the circuit.


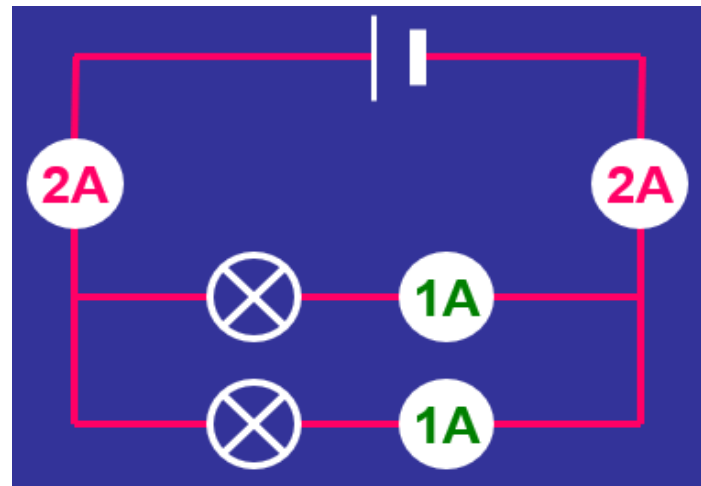
## Parallel Circuit

Current is shared between the components.



# Voltage, Current & Power

- One Volt is a Joule per Coulomb (J/C)
- One Amp of current is one Coulomb per second ( $6.24 \times 10^{18}$  electrons/second).
- If I have one volt (J/C) and one amp (C/s), then multiplying gives Joules per second (J/s). I.e. Power: J/s = Watts
- The formula for electrical power is:
  - $P$  (power) =  $V$  (voltage) x  $I$  (current)